
## **SS-Type Wireless Power Transfer**

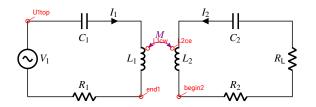

Resonant frequency f, angular frequency  $\omega$ :

$$f = \frac{1}{2\pi\sqrt{L_1C_1}} = \frac{1}{2\pi\sqrt{L_2C_2}}$$
$$\omega = 2\pi f$$

Equivalent resistance:

$$Z_{in1} = R_1 + \frac{\omega^2 M^2}{R_2 + R_e}$$

$$Z_{in2} = j \left[ \omega M + \frac{R_1 (R_2 + R_e)}{\omega M} \right]$$
 $\approx j \omega M$ 

Inverter output voltage  $V_1$ , rectifier input voltage  $V_2$ :

$$Z_{in1} = R_1 + \frac{\omega^2 M^2}{R_2 + R_e}$$

$$V_1 \approx \frac{4}{\pi} V_{DC} \sin(\omega t) = 1.27 V_{DC} \sin(\omega t)$$

$$V_2 = R_e I_2 = \frac{4R_e V_{DC} \cos(\omega t)}{\pi \left[\omega M + \frac{R_1(R_2 + R_e)}{\omega M}\right]}$$

$$\approx \frac{4R_e}{\pi \omega M} V_{DC} \cos(\omega t)$$

Current:


$$\begin{split} I_1 &= \frac{V_1}{Z_{in1}} = \frac{4V_{\text{DC}}\sin(\omega t)}{\pi \left(R_1 + \frac{\omega^2 M^2}{R_2 + R_e}\right)} \\ I_2 &= \frac{V_1}{Z_{in2}} = \frac{4V_{\text{DC}}\cos(\omega t)}{\pi \left[\omega M + \frac{R_1(R_2 + R_e)}{\omega M}\right]} \approx \frac{4}{\pi \omega M} V_{\text{DC}}\cos(\omega t) \end{split}$$

Note:  $I_2$  is constant with respective to different  $R_L$  since  $R_1 \approx 0$ .

## **RMS** value

$$V = V_m \sin(\omega t)$$
 
$$V_{\mathsf{RMS}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2 \, \mathrm{d}t} = \frac{V_m}{\sqrt{2}}$$

## **Phsae Shift Control**

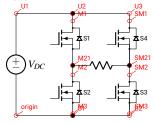


$$S_{1} = \bar{S}_{2} = \frac{1}{2} \left\{ \text{sign} \left[ \sin \left( \omega t + \frac{D}{2} \pi - \frac{2\pi}{4} \right) \right] + 1 \right\}$$

$$S_{3} = \bar{S}_{4} = \frac{1}{2} \left\{ \text{sign} \left[ \sin \left( \omega t - \frac{D}{2} \pi - \frac{2\pi}{4} \right) \right] + 1 \right\}$$

$$V_{R} = V_{DC}(S_{1} - S_{3}) \approx \frac{4}{\pi} V_{DC} \sin \left( D \frac{\pi}{2} \right) \sin(\omega t)$$

## **Full Bridge Rectifier**

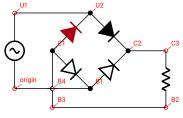

Average output voltage:

$$V_{ave} = \frac{1}{\pi} \int_{\alpha}^{\pi} \sqrt{2} V_s \sin(\omega t) d(\omega t) = \frac{2\sqrt{2} V_s}{\pi} \frac{1 + \cos \alpha}{2}$$